ESP P3a Class AB Audio Power Amplifier

From Reverse Engineering to High-Fidelity Sound

A personal journey into mastering analog signal amplification



Designed by Rod Elliott, Reverse Engineered by Mukhtar Suleman


Architecture & Design Choice

The goal was to design and prototype a **100W Class AB audio amplifier** for high-fidelity speaker output — combining **clean sound** with **efficient power delivery**.

After evaluating amplifier topologies:

- Class A offers excellent linearity but is highly inefficient (~25%).
- Class B improves efficiency (~78%) but suffers from crossover distortion.
- Class AB strikes a balance by using diode or V_BE biasing, both output transistors remain slightly on, reducing distortion and preserving efficiency.

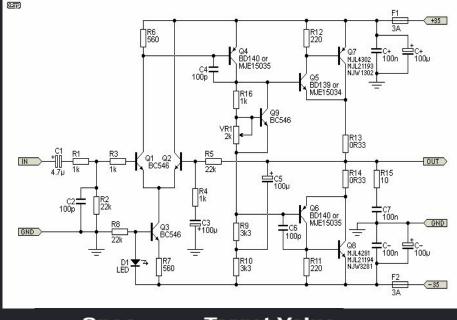I chose to reverse engineer **Rod Elliott's ESP P3a design** due to its clean schematic layout, thermal stability, and proven high-fidelity performance — making it ideal for hands-on prototyping and learning.



Spec	Target Value
Output Power	100W @ 4Ω
Voltage Rails	±35V
Frequency Response	20Hz–20kHz
THD+N	< 0.1%
Application	Home Stereo Audio

ESP P3A Design Requirements & Specifications

Lor For Design Requirements & opecifications		
Parameter	Specification	
Power Output	60–100 W RMS per channel	
Load Impedance	8Ω (±42 V rails) or 4Ω (±35 V rails)	
Supply Voltage (Rails)	$\pm 35 V$ for 4 Ω loads; $\pm 42 V$ for 8 Ω loads	
THD+N	< 0.05% at 1 kHz, full power	
Frequency Response	10 Hz – 100 kHz (–1 dB)	
Slew Rate	20 V/μs	
Thermal Considerations	Large heatsink required; bias transistor mounted on heatsink for thermal tracking	
Stability	Stable with capacitive loads; phase margin > 45°; gain margin > 10 dB	
Application	Hi-Fi stereo, bi-amp systems, instrument amplifiers	


Class AB Topology Explanation


Behavior Summary:

- At Vin = 0V
 - \rightarrow Both NPN and PNP slightly conduct \rightarrow no distortion at zero-crossing.
- 1. Vin > 0 (Positive Half)
 - \rightarrow NPN turns on more \rightarrow sources current to the load.
 - → PNP turns off gradually.
- 2. Vin < 0 (Negative Half)
 - → PNP turns on more → sinks current from the load.
 - → NPN turns off gradually.

Mitigating Crossover Distortion:

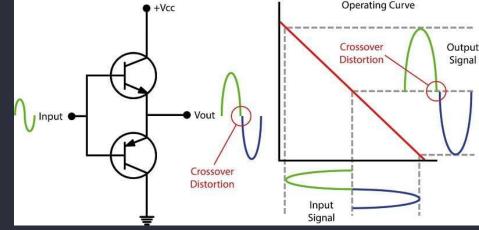- V_BE multiplier creates a modest quiescent current (typically 50–100 mA per output transistor), just enough to avoid distortion without excessive heat.



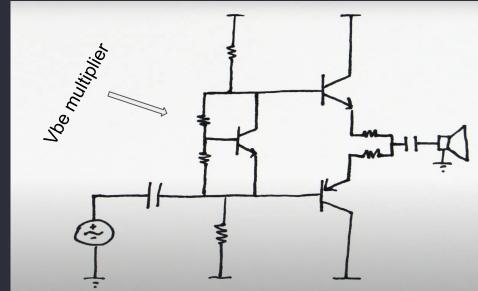

R2, R3, R4, R5 **Tail Current** Q3, D1, R7 Source Voltage Q4, Q5, R16, **Amplification** C4 Stage (VAS) **Bias Control** Q9, VR1, (V_BE R16 Multiplier) **Output Stage** Q6, Q7, Q8, (Class AB) R13, R14, **C7** Feedback & OUT node \rightarrow **Output** R15, C7, **Filtering** trace back to R2


Block

Input Stage

Components

Q1, Q2, R1,

ESP P3a schematic

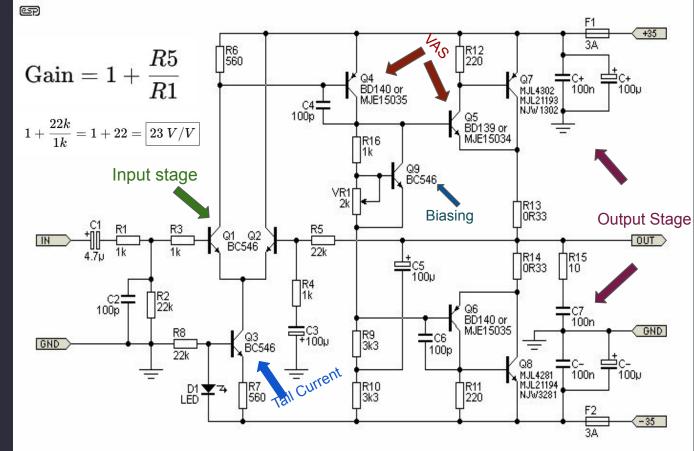

Simulation & Validation Process

I simulated the ESP P3a input stage in LTSpice to validate the differential pair's behavior.

To isolate the stage, I disconnected the feedback loop from Q2's base.


I applied a 1.5V AC signal to Q1's base to mimic an audio input.


The tail current source uses a white LED (3.2V) and BJT with a 470Ω emitter resistor:


- Tail current ≈ (3.2V 0.7V) / 470Ω ≈ 5.3 mA
- ≈ 2.65 mA per transistor

Transconductance: $g \square \approx 2.65 \text{ mA} / 25 \text{ mV} = 0.106 \text{ S}$

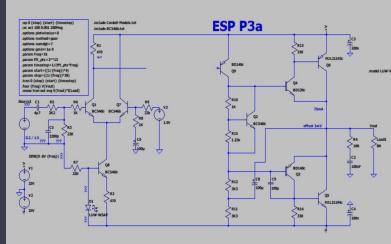Voltage gain: A ≈ g □ × RC = 0.106 × 470 ≈ 49.8 V/V (~34 dB)



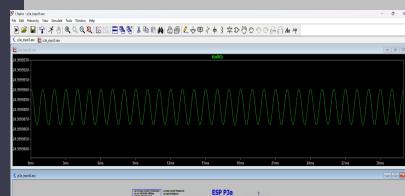

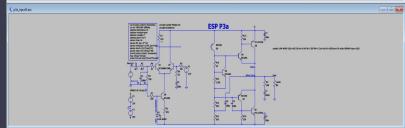

Simulation & Validation Process

Voltage gain stage (VAS) and Class AB driver components now added


Q4 and Q5 form the core of the gain stage:

- Q4 acts as the current source load.
- Q5 operates as the voltage amplification stage (VAS), boosting the signal from the input stage.

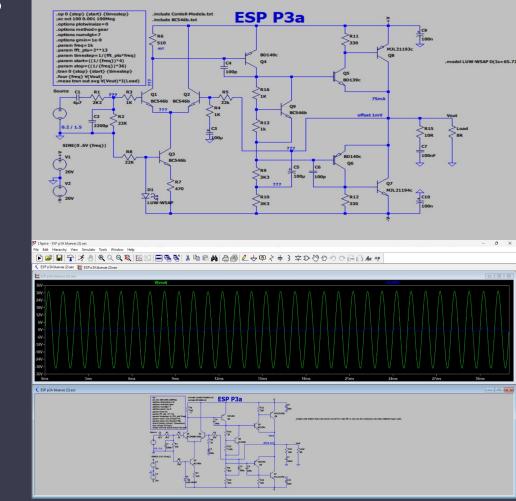Q5 also drives the PNP transistor (Q8) — the upper half of the Class AB output stage.


The Class AB output biasing is controlled by Q9, which is configured as a VBE multiplier

- This sets the quiescent current between Q8 (PNP) and Q6 (NPN), helping to minimize crossover distortion
- 30Vpp > 21.2Vrms > P = (21.2)^2/8 = 56.2W or P = (21.2)^2/4 = 112.4W





Simulation Results (LTSpice) Gain:Vout /Vin 30V/1.5 = 20Direct Newton iteration for .op point succeeded. N-Period=1 Fourier components of V(vout) DC component: -0.0572217 Harmonic Normalized Frequency Fourier Number [Hz] Component Component 1.000e+3 3.130e+1 1.000e+0 ESP p3A bluevas (2).as 2.000e+3 2.074e-3 6.627e-5 3.000e+3 1.728e-3 5.522e-5 2.778e-4 4.000e+3 8.876e-6 5.000e+3 1.271e-4 4.061e-6 6.000e+3 1.122e-4 3.586e-6 7.000e+3 2.221e-5 7.098e-7 3.683e-5 8.000e+3 1.177e-6 9.000e+3 1.813e-5 5.795e-7 Partial Harmonic Distortion: 0.008690% Total Harmonic Distortion: 0.008694% THD Frequency response

FFT

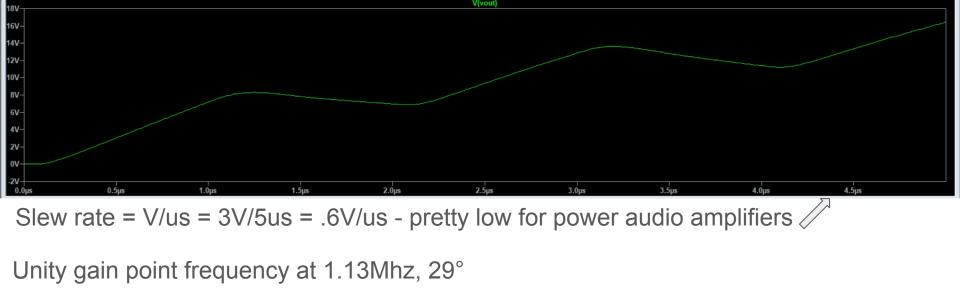



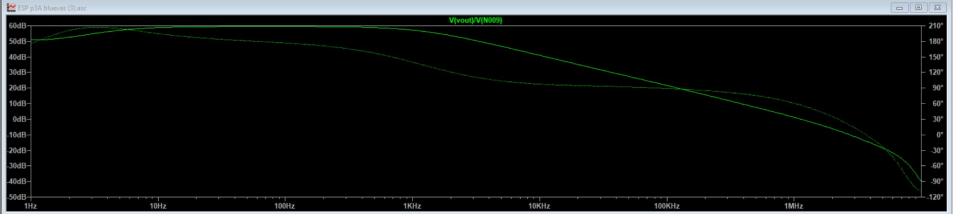

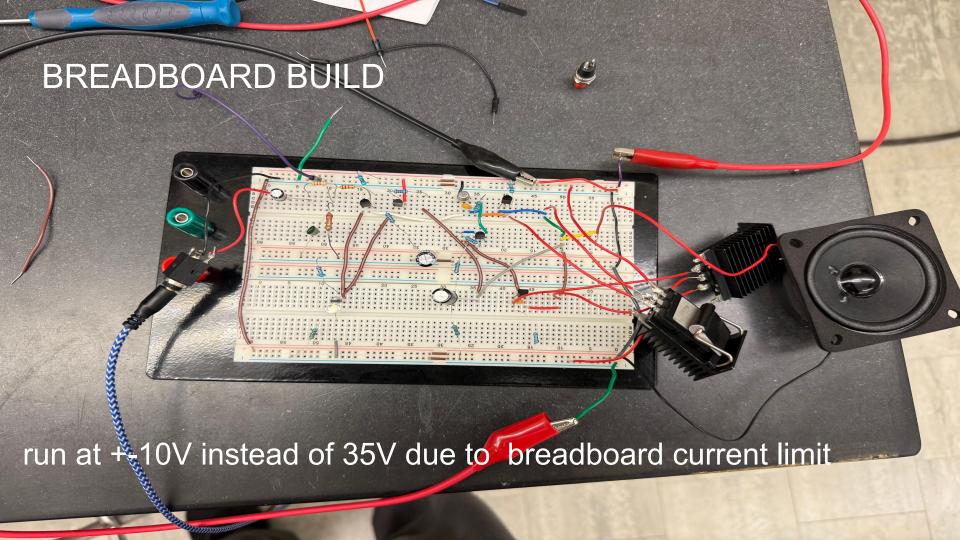

What I could still validate at ±10V

<u>Test/Observation</u>	What It Confirms
DC operating points	Biasing of all transistors (VAS, differential pair, output)
Quiescent current	V BE multiplier working, output stage not oscillating
Small-signal gain	Expected voltage gain (still close to 20×, scaled output)
Waveform symmetry	Output is centered at 0V, no major offset
Crossover distortion check	Class AB smooth zero-crossing behavior
Stability	No self-oscillation at idle or with input signal

Breadboard Results


Input signal: sine 350mV 1khz yellow probe

Output: 7.60V blue probe


Gain = $7.6/.35 = 21.7V/V \approx 23V/V$

https://youtube.com/shorts/S-6Zr4V4KZq?si=dZFbJqk70pWXQKoZ

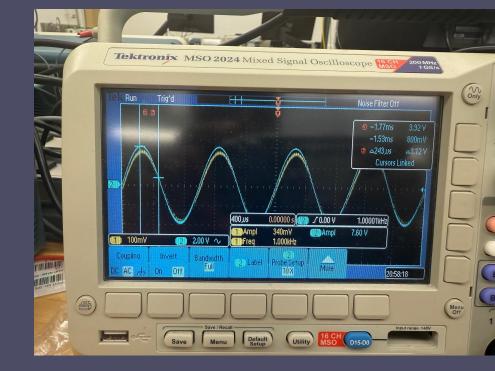
https://www.youtube.com/watch?v=ZeihuCMit3U



PCB Schematic

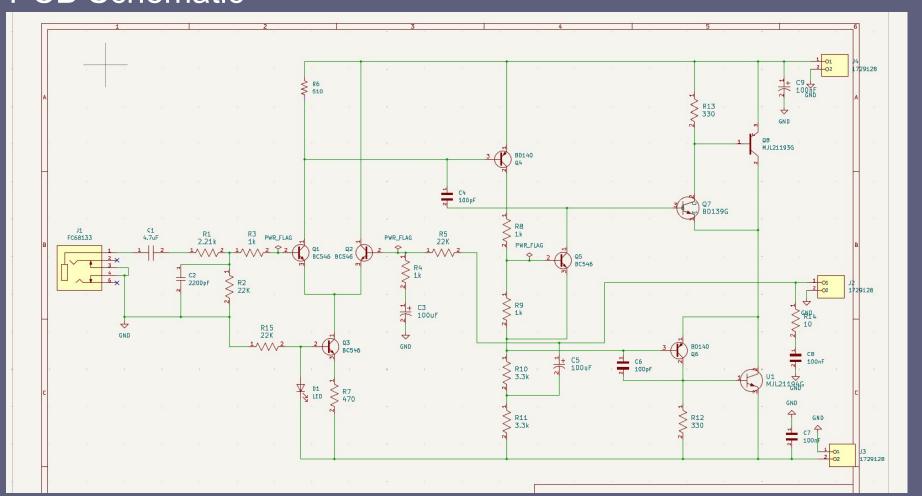

PCB

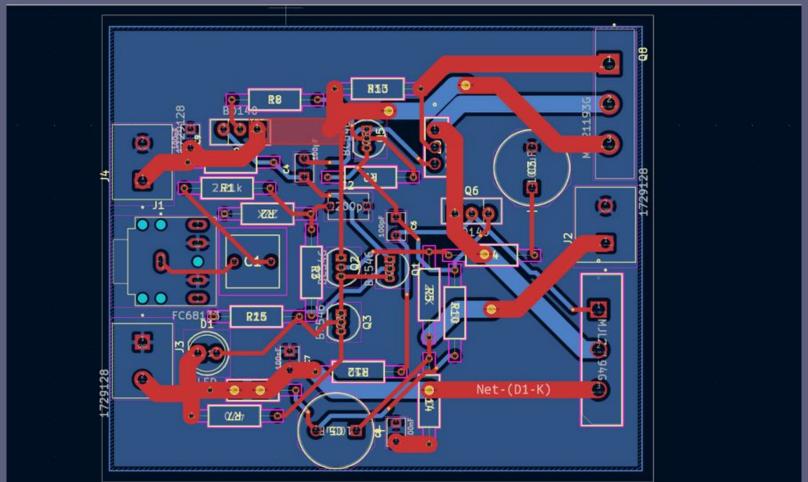

3D PCB


Software: KiCad 7.0

Layers: 2-layer board

Copper Weight: 1 oz

(35µm)

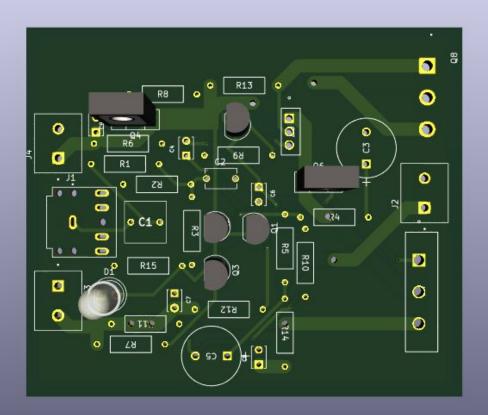Trace Width for Power Rails: 2.3 mm (Handles >3A for output stage and speaker drive)





Lessons Learned – ESP P3a Class AB Amplifier

1. PCB Layout is Everything

 High-current traces need to be treated like copper busbars — used 2.3 mm traces for >3A paths (Q7/Q8 → Vout → Load)

2. Simulation vs. Reality

- Simulations in LTSpice showed ideal THD, slew rate, and stability
- Breadboard testing (±10V rails) revealed subtle distortion and thermal drift
- 3. Real analog design is about **debugging what simulation missed**
 - Building first at reduced voltage on breadboard is underrated
 - Every trace has a story and analog layout is as much an art as a science

Cites

https://sound-au.com/project3a.htm